

Electric potential : — ^{constant of} the electric potential or voltage at any point in an electric field is equal to the work done in moving a unit positive charge from infinity to that point against the electric field. The unit of electric potential is volt (V).

Potential difference : — The potential difference betⁿ two points in an electric field is equal to the work done in moving a unit positive charge from the point of lower potential to the point of higher potential. The unit of potential difference is volt.

Electromotive force (emf) : — The difference of potential produced by sources of electric energy which can be used to drive currents through external circuits.

Current : — An electric current is said to flow through a conductor when there is a

The unit of current is Ampere.

Source :- An active pair of terminals that can deliver power to a load.

Load :- The rate at which energy is fed into a process or removed from it. The examples of electrical loads are TV, cooler, bulb, fan, breeze, etc.

Resistance :- The resistance is the property of a material by virtue of which it opposes the flow of current through it. The unit of resistance is Ohm (Ω).

The resistance of a conducting wire is directly proportional to its length (l) ; It is inversely proportional to its area of cross-section (a). It depends upon the nature of the conducting material. Also, it depends upon temperature. Mathematically,

$$R \propto \frac{l}{a}$$

where ρ (rho) is a constant of material called specific resistance or resistivity. It $l = 1m$ and $a = 1m^2$ then $\rho = R$. So, the resistivity of a material is the resistance offered by $1m$ of its length Δ having a cross-section of $1m^2$.

The SI unit of specific resistance is Ohm-metre. The reciprocal of resistance is called conductance (G). Mathematically,

$$G = \frac{1}{R}$$

The unit of conductance is Ohm⁻¹ or mho.

OHM'S LAW :- The Ohm's law is defined as follows.

The current passing through a conductor is directly proportional to the potential difference across the ends of the conductor, provided the physical condition of the conductor remains the same. Mathematically,


$$I \propto V$$

$$\Rightarrow \frac{I}{V} = \text{constant} = R$$

$$R = \frac{V}{I}$$

where, the constant 'R' is the resistance of the conductor.

conductors in series:-

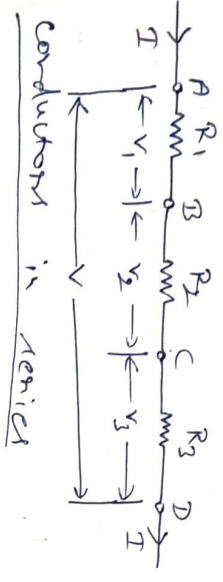

If the conductors are connected end to end, and same current flows through all conductors and p.d. across each one is different depending upon their resistances, then the conductors are said to be connected in series.

In the above fig, A and D are the free ends of three conductors AB, BC & CD connected in series. Let R_1, R_2 & R_3 be the respective resistances. Let R = resistance of combination. V = total p.d. across the resistors. I = current.

$$V = IR \quad (1)$$


But $V = \sum$ of the individual p.d. across R_1, R_2 & R_3 .
 $V = V_1 + V_2 + V_3$

$$= IR_1 + IR_2 + IR_3 \dots (2)$$

By putting the value of 'V' from eqn (1) in eqn (2), we get
 $IR = IR_1 + IR_2 + IR_3$

$$\Rightarrow R = R_1 + R_2 + R_3 \dots (3)$$

conductors in parallel:-

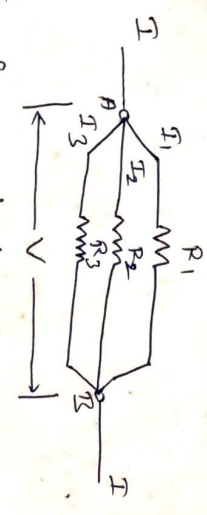

If the conductors are connected across two common points, they are said to be connected in parallel. In the above fig, R_1, R_2 & R_3 are connected between the common points A and B. So, same p.d. (V) exists between the ends of each conductor.

The current passing through each is different depending upon their resistances. Let the main current I is divided into I_1, I_2 & I_3 through the resistors R_1, R_2 & R_3 respectively. If R is the combined resistance between A & B, then

$$I = \frac{V}{R} \quad (1)$$

Again $I = I_1 + I_2 + I_3$

$$\Rightarrow I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \dots (2)$$


on putting the value of I from

eq (1) in eq (2), we get

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

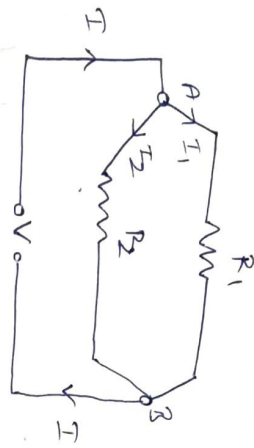Division of current in parallel circuits:



(Two resistors in parallel across a voltage V)

Let's consider two resistors joined in parallel across a voltage V . So,

current in branches $I_1 = \frac{V}{R_1}$ & $I_2 = \frac{V}{R_2}$

$$\frac{I_1}{I_2} = \frac{V}{R_1} \div \frac{V}{R_2}$$

$$= \frac{V}{R_1} \times \frac{R_2}{V}$$

$$= \frac{R_2}{R_1}$$

So, the division of current in the

branches of a parallel circuit is

inversely proportional to their resistance.

Again, $I_1 + I_2 = I$

$$\Rightarrow I_2 = I - I_1$$

$$\frac{I_1}{I - I_1} = \frac{R_2}{R_1}$$

$$\Rightarrow I_1 R_1 = R_2 (I - I_1)$$

$$\Rightarrow I_1 R_1 = R_2 I - R_2 I_1$$


$$\Rightarrow I_1 R_1 + R_2 I_1 = R_2 I$$

$$\Rightarrow I_1 (R_1 + R_2) = R_2 I$$

$$\Rightarrow I_1 = I \times \frac{R_2}{(R_1 + R_2)}$$

$$\text{And } I_2 = \frac{I R_1}{(R_1 + R_2)}$$

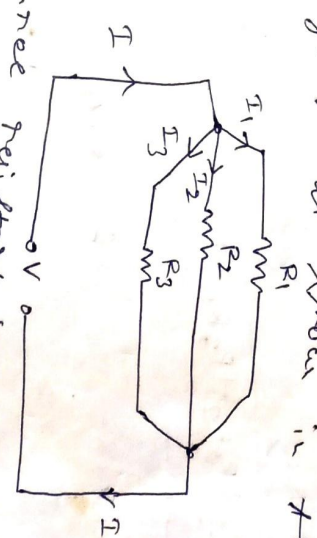Let's consider three resistors R_1, R_2 & R_3 joined in parallel across a voltage V as shown in the fig below.



(Three resistors in parallel across a voltage V).

Then, $I = I_1 + I_2 + I_3$

Let $R =$ equivalent resistance of

$$R_1 || R_2 || R_3$$

$$V = IR = I_1 R_1 = I_2 R_2 = I_3 R_3$$

$$\text{So, } \frac{I}{I_1} = \frac{R_1}{R}$$

$$\Rightarrow I_1 = \frac{IR}{R_1}$$

$$\text{Similarly, } I_2 = \frac{IR}{R_2} \quad \& \quad I_3 = \frac{IR}{R_3}$$

But $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$
 $= \frac{R_2 R_3 + R_3 R_1 + R_1 R_2}{R_1 R_2 R_3}$
 $\Rightarrow R = \frac{R_1 R_2 R_3}{R_2 R_3 + R_3 R_1 + R_1 R_2}$

So,

$I_1 = I \left(\frac{R_2 R_3}{R_2 + R_3 + R_1} \right)$

$I_2 = I \left(\frac{R_3 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right)$

$I_3 = I \left(\frac{R_1 R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right)$

Electric power, —

Electric power is the rate of doing work.

Mathematically, $P = VI$

where, $P = \text{Power}$

$V = \text{Voltage}$

$I = \text{Current}$

(a) Power in series circuit: —

(i) The reciprocal of total power supplied by the source in any series resistive circuit is equal to the sum of the reciprocals of power in each resistor in series.

$\frac{1}{P_s} = \frac{1}{P_1} + \frac{1}{P_2} + \frac{1}{P_3} + \dots + \frac{1}{P_n}$

where, $P_n = \text{power in the last resistor in series}$

$n = \text{no. of resistors in series}$

$P_1, P_2, P_3, \dots = \text{powers in the resistors of the series circuit supplied by source}$

(ii) The total power in the series circuit is the total voltage applied to a circuit multiplied by the total current.

Mathematically,

$P_s = V_s I = I^2 R_T = \frac{V_s^2}{R_T}$

where, $V_s = \text{total voltage applied}$

$R_T = \text{total resistance}$

$I = \text{total current}$

(b) Power in parallel circuit: —


The total power supplied by the source in any parallel resistive circuit is equal to the sum of the powers in each resistor in parallel, i.e.,

$P_s = P_1 + P_2 + P_3 + \dots + P_n$

$n = \text{no. of resistors in parallel}$

$P_s = \text{total power supplied by source}$

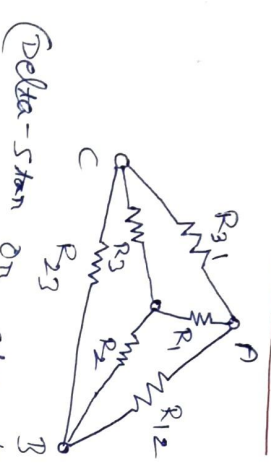$P_1, P_2, P_3, \dots, P_n = \text{powers in the resistors of the parallel circuit}$



(Delta-Star or Star-Delta transformation)

Let's consider a delta ckt ABC made up of three resistors R_{12} , R_{23} & R_{31} as shown above. Let its equivalent ckt is R_1 , R_2 & R_3 . The resistance bet terminals A and B is delta connection

$$= \frac{R_{12} \times (R_{23} + R_{31})}{R_{12} + (R_{23} + R_{31})} \quad \dots (1)$$

The resistance bet terminals A and C in the star connection

$$= R_1 + R_2 \quad \dots (2)$$

Because the terminals are same, so

$$R_1 + R_2 = \frac{R_{12} \times (R_{23} + R_{31})}{R_{12} + (R_{23} + R_{31})} \quad \dots (3)$$

In the same way, by solving the terminals B and C, and A, we get

$$R_2 + R_3 = \frac{R_{23} \times (R_{31} + R_{12})}{R_{23} + (R_{31} + R_{12})}$$

$$R_3 + R_1 = \frac{R_{31} \times (R_{12} + R_{23})}{R_{31} + (R_{12} + R_{23})} \quad \dots (4)$$

Now, by subtracting eqn (4) from eqn (3) and adding the result to eqn (5), we get

$$R_1 + R_2 - (R_2 + R_3) + R_3 + R_1 =$$

$$\frac{R_{12} \times (R_{23} + R_{31})}{R_{12} + (R_{23} + R_{31})} - \frac{R_{23} \times (R_{31} + R_{12})}{R_{23} + (R_{31} + R_{12})}$$

$$+ \frac{R_{31} \times (R_{12} + R_{23})}{R_{31} + (R_{12} + R_{23})}$$

$$R_3 + R_1 =$$

$$\Rightarrow R_1 + R_2 - R_2 - R_3 + R_3 + R_1 =$$

$$\frac{R_{12} R_{23} + R_{12} R_{31} - R_{23} R_{31} - R_{23} R_{12} + R_3 R_{12} + R_3 R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$\Rightarrow 2R_1 = \frac{2R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$\Rightarrow R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$


In the same way, we get

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}}$$

Delta transformation

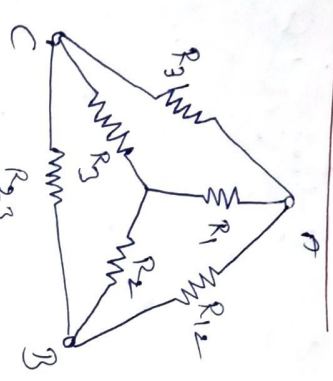

(delta - star on star-delta transformation)

It is a method of obtaining equivalent delta or a star. The total resistance between A and C must be same for both star and delta connections. So,

$$R_2 + R_3 = R_{23} \parallel (R_{31} + R_{12})$$

$$= \frac{R_{23} \cdot (R_{31} + R_{12})}{R_{23} + R_{31} + R_{12}} \quad \dots (1)$$

Similarly, we get

$$R_3 + R_1 = R_{31} \parallel (R_{12} + R_{23})$$

$$= \frac{R_{31} \cdot (R_{12} + R_{23})}{R_{31} + R_{12} + R_{23}} \quad \dots (2)$$

$$R_1 + R_2 = R_{12} \parallel (R_{23} + R_{31})$$

$$= \frac{R_{12} \cdot (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad \dots (3)$$

$$2(R_1 + R_2 + R_3) = 2 \frac{(R_{23} \cdot R_{31} + R_{31} \cdot R_{12} + R_{12} \cdot R_{23})}{R_{12} + R_{23} + R_{31}} \quad \dots (4)$$

$$\Rightarrow R_1 + R_2 + R_3 = \frac{R_{23}R_{31} + R_{31}R_{12} + R_{12}R_{23}}{R_{12} + R_{23} + R_{31}} \quad \dots (4)$$

By subtracting eqn (1) from eqn (4), we get

$$R_1 + R_2 + R_3 - (R_2 + R_3) = \frac{R_{23}R_{31} + R_{31}R_{12} + R_{12}R_{23}}{R_{12} + R_{23} + R_{31}} - \frac{(R_{23}R_{31} + R_{23}R_{12})}{R_{23} + R_{31} + R_{12}}$$

$$\Rightarrow R_1 = \frac{R_{23}R_{31} + R_{31}R_{12} + R_{12}R_{23} - R_{23}R_{31} - R_{23}R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$= \frac{R_{31}R_{12}}{R_{12} + R_{23} + R_{31}} \quad \dots (5)$$

By subtracting eqn (2) & (3) from eqn (4), we get

$$R_2 = \frac{R_{12}R_{23}}{R_{12} + R_{23} + R_{31}} \quad \dots (6)$$

$$R_3 = \frac{R_{23}R_{31}}{R_{12} + R_{23} + R_{31}} \quad \dots (7)$$

By dividing eqn (5) by eqn (6), we get

$$\frac{R_1}{R_2} = \frac{R_{31}}{R_{12}} \quad \dots (8)$$

$$\Rightarrow R_{31} = \frac{R_1 \times R_{12}}{R_2} \quad \dots (8)$$

Similarly, we get

$$\frac{R_3}{R_1} = \frac{R_2}{R_2} \quad \text{on } R_{12} = \frac{R_1 \cdot R_2}{R_3} \quad (9)$$

By substituting the values of

R_{31} & R_{12} from eqn (8) and

eqn (9) respectively in eqn (1), we get

$$R_2 + R_3 = R_2 \left(R_1 \cdot \frac{R_2}{R_3} \right) + R_2 \left(R_1 \cdot \frac{R_2}{R_3} \right)$$

$$\Rightarrow R_2 + R_3 = \left(R_1 \cdot \frac{R_2}{R_3} \right) + \left(R_1 \cdot \frac{R_2}{R_3} \right)$$

$$= \left(\frac{R_1 \cdot R_2}{R_3} + \frac{R_1 \cdot R_2}{R_3} \right) \cdot \frac{1 + (R_1/R_2) + (R_1/R_3)}$$

$$= \left(\frac{R_1 \cdot R_2}{R_3} \cdot R_2 + R_1 \cdot R_2 \cdot R_2 \right) \cdot \frac{1 + (R_1/R_2) + (R_1/R_3)}{R_2 \cdot R_3}$$

$$= \frac{R_1 \cdot R_2 \cdot R_2 + R_1 \cdot R_2 \cdot R_2}{R_2 \cdot R_3 + R_1 \cdot R_3 + R_1 \cdot R_2}$$

$$= \frac{R_2 \cdot R_3 + R_1 \cdot R_3 + R_1 \cdot R_2}{R_1 \cdot R_2 \cdot (R_2 + R_3)}$$

$$\Rightarrow R_1 \cdot R_2 \cdot (R_2 + R_3) = R_2 \cdot R_3 + R_1 \cdot R_3 + R_1 \cdot R_2$$

$$\Rightarrow R_2 = R_2 + R_3 + R_2 R_3 / R_1$$

Similarly, we get

$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

Superposition Theorem

Thevenin's Theorem:-

In a network of linear resistors

containing more than one source, the

resultant current on any branch, the

in an element is found by considering

one source at a time, and all

other sources replaced temporarily

by their internal resistances, followed

by adding the currents on entry

due to the individual sources.

Thevenin's Theorem:-

The Thevenin's theorem is derived

as the current flowing through a

resistance R_L connected across any

two terminals of a network containing

one or more sources of current on

voltage given by

$$I = \frac{V_{Th}}{R_L + R_{Th}}$$


where $V_{TL} =$ open circuit voltage with R_L disconnected.

$R_{TL} =$ equivalent resistance or the network with R_L removed and the sources replaced by their respective internal resistances.
Maximum Power Transfer Theorem: -

It states that maximum power output from a network is obtained when the load resistance is equal to Thevenin's equivalent resistance of the network as seen from the load terminals.
Kirchoff's first law or Kirchoff's current law (KCL): -

This law states that in any network of conductors in any circuit, the algebraic sum of electrical current in all the conductors meeting at any point is zero.

Illustration: -

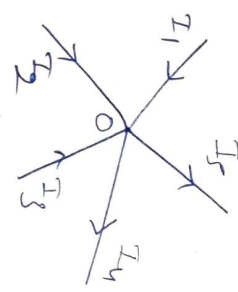

Let there be a no. of conducting elements meeting a junction 'O' as shown above. Let the incoming currents I_1, I_2 & I_3 are positive, I_4 as negative.

Outgoing currents I_4 & I_5 will be negative. According to KCL,


$$I_1 + I_2 + I_3 - I_4 - I_5 = 0$$

$$\Rightarrow I_1 + I_2 + I_3 = I_4 + I_5$$

Kirchoff's second law or Kirchoff's mesh or voltage law (KVL): -

This law states that the algebraic sum of the products of current and resistance of each conductor in any closed path in a network plus the algebraic sum of the voltages in that path is zero. Mathematically,
$$\sum IR + \sum V = 0$$

Illustration: -

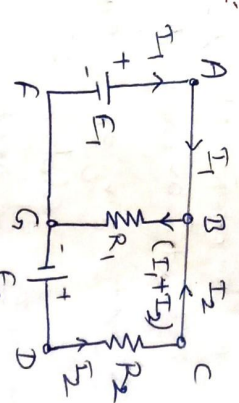

Let's consider the network as shown above. Let's consider the loop FABGF. By applying KVL to it, we get

$$E_1 + (-)(I_1 + I_2)R_1 = 0$$

$$\Rightarrow E_1 = (I_1 + I_2)R_1$$

By applying KVL to loop BCDGB, we get

$$\Rightarrow E_2 = I_2 R_2 + (I_1 + I_2)R_1$$

Fleming's Right Hand Rule - It states that whenever

the number of magnetic lines of force passing through a circuit changes, an induced e.m.f. is set up in the circuit.

Fleming's Second Law of Electromagnetics

Induction: - It states that the magnitude of the induced e.m.f. is proportional to the rate of change of magnetic lines of force. Mathematically,

$$e = -N \frac{d\phi}{dt} \text{ volt.}$$

Fleming's Left-Hand Rule: - Hold


the thumb, the first finger and the middle finger of the left hand at right angles to each other. If the first finger points to the direction of field, the middle finger to the direction of the current, then thumb points to the direction of motion or force.

Fleming's Right Hand Rule: - Hold the thumb, the first and the middle fingers of the right hand at right angles to each other. If the thumb points to the direction of motion or force,

the first and the middle fingers of the right hand at right angles to each other. If the thumb points to the direction of motion or force,

the first finger to the direction of the field, then the middle finger points to the direction of the induced e.m.f.

Generation of alternating e.m.f.:

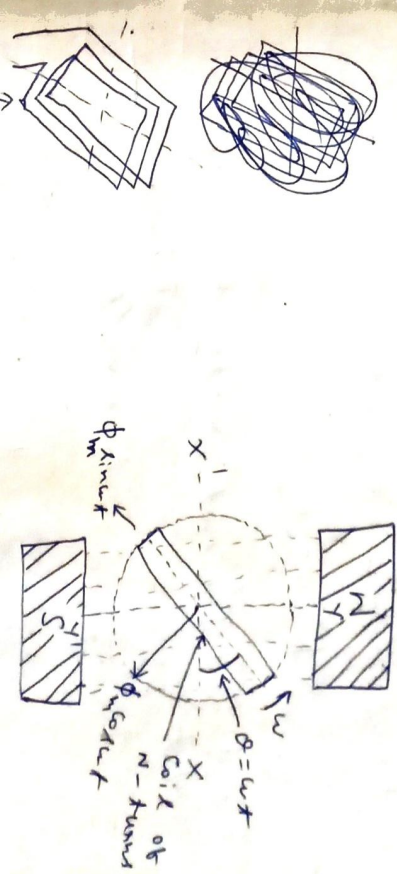

Rectangular coil of N-turns and area $A \text{ m}^2$ cross section $A \text{ m}^2$
Let's consider a rectangular coil of N turns and area $A \text{ m}^2$ rotating in a uniform magnetic field with an angular velocity ω radian/sec about X-axis in its own plane. Suppose ϕ_m is the max flux density perpendicular to the axis of rotation when the plane of the coil coincides with the X-axis. Let θ be the angle between the normal to the coil's area and the X-axis.

Let θ be the angle between the normal to the coil's area and the X-axis. The induced e.m.f. is given by $e = -N \frac{d\phi}{dt}$. The flux $\phi = B A \cos \theta$. The induced e.m.f. is $e = N B A \omega \sin \theta$. The induced e.m.f. is a sine wave.

position the flux component to the 'pole' of the coil, so, the flux linkage of the coil in this position is $N\phi = N\phi_{\text{cos}\theta}$

The instantaneous induced e.m.f. at time when $\theta = \omega t$ is

$$e = -\frac{d}{dt}(N\phi) \text{ volt}$$

$$= -\frac{d}{dt}(N\phi_{\text{cos}\theta}) \text{ volt}$$

$$= -N\phi_m \left(\frac{d}{dt} \text{cos}\theta \right) \text{ volt}$$

$$= -N\phi_m \times \left\{ -\text{sin}\theta \times \frac{d}{dt}(\omega t) \right\} \text{ volt}$$

$$= \omega N\phi_m \text{sin}\theta \text{ volt} \dots (1)$$

The induced e.m.f. has a maximum value of E_m when $\text{sin}\theta = \text{sin}90^\circ = 1$.

So, $E_m = \omega N\phi_m \text{ volt} = \omega N B_m A \text{ volt}$

$$= 2\pi f N B_m A \text{ volt} \dots (2)$$

where, $f =$ the no. of revolutions/sec

$B_m =$ max flux density in henry



From eqns (1) & (2), we get

$$e = E_m \text{sin}\theta = E_m \text{sin}\omega t \text{ volt} \dots (3)$$

The current 'i' at any time the coil is proportional to the induced e.m.f. in the coil

So, the induced alternating current $i = I_m \text{sin}\omega t$ ampere $\dots (4)$

where $I_m =$ max value of the current

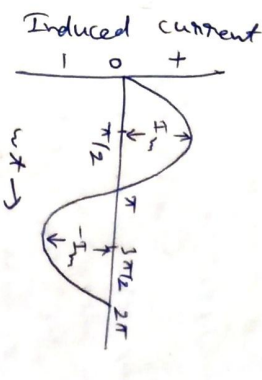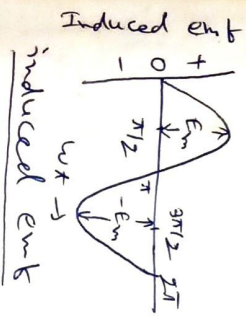

Difference betn

Alternating current

1) Both voltage and current reverses periodically.

2) Low cost of production.

3) An a.c. generator is almost free from dissipation of energy.

4) The cost of transmitting a.c. power can be reduced by using step-up transformers.

5) By using transformers a.c. voltage can be lowered or raised as desired.

6) A.c. ckt current can be decreased by using choke or capacitor without any appreciable power loss.

7) A.c. can be converted into D.C. by using a device called converter.

Direct current

1) Both voltage and current remain constant.

2) Higher cost of production

3) A D.C. generator undergoes dissipation of energy.

4) No such provision can be made.

5) No such provision can be made.

6) For decreasing D.C. ckt current a resistor has to be used where power dissipation becomes large.

7) D.C. can be converted to a.c. by using inverter.

D.C. & A.C. :-

⑧ H.C. can't be used directly for electroplating, electrotyping, etc.

⑨ A.C. motors and other appliances are more robust and durable.


⑩ A.C. attracts a person. So, faulty insulation of a.c. are more dangerous. Because peak of a.c. is $\sqrt{2}$ times its effective value.

⑪ D.C. gives a repelling shock to a person. So, faulty insulation of D.C. are less dangerous.

Direct Current: - A current which maintains a constant direction, i.e., current which flows in one direction only. Although, it may have appreciable fluctuations in its magnitude.

Alternating current: - An alternating current is one that reverses periodically in direction and whose magnitude undergoes a definite cycle of changes in definite intervals of time.

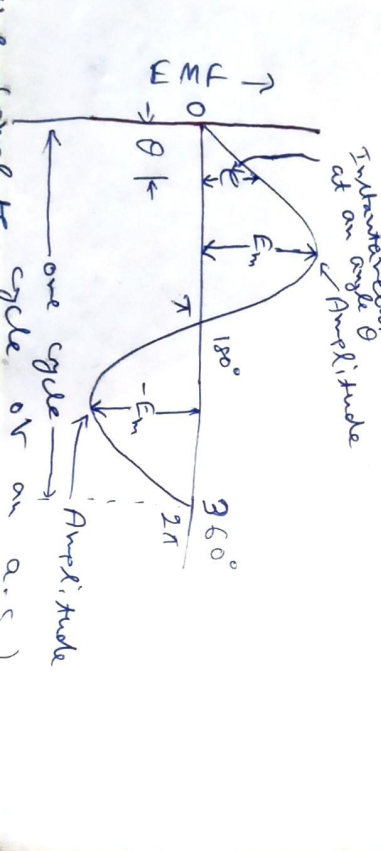A.C. Terms: -
 Instantaneous value
 at an angle θ
 Amplitude



cycle: - The cycle is one complete set of positive, zero and negative values of an alternating quantity.

Amplitude on peak value: - It is the maximum value, positive or negative, of an alternating quantity.

Instantaneous value: - The instantaneous value of an alternating quantity is its value at any instant.

Time period (T): - It is the duration of time required for an a.c. quantity to complete one cycle.

Frequency (f): - It is the number of cycles that occurs in one second.

The unit of frequency is the Hertz (Hz) or cycles/sec. mathematically

$$f = \frac{1}{T}$$

or, $T = \frac{1}{f}$

Phase: - The phase of an alternating quantity is the fraction of the period on cycle that has elapsed since it last passed through the zero position or origin.

Phase angle (phi): - The phase angle phi is equivalent of phase in radians or degrees.

Phase difference: - It is the angular

Quantities.

Average or mean value: - It is the arithmetic sum of all the values divided by the total number of value used to obtain the sum. The average value of any cycle of wave form is area under the wave form divided by time period.

The average value of current (I_{av}) of an a.c. sinusoidal wave is

$$I_{av} = \frac{2I_m}{\pi} = 0.637 I_m$$

where, I_m = Maximum value of current
Root mean Square (RMS) or effective value

It is the square root of average value of square of alternating quantity over a time period. The rms value of a.c. current is equivalent direct flow through a given circuit from a given time produces the same amount of heat as produced by the alternating current when allowed to flow through the same circuit for the same time. The rms value of a.c. sinusoidal current (I_{rms})

$$I_{rms} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$$

where I_m = Maximum value of current
Form factor (K_f): - It is the ratio of rms value to the average value of an alternating quantity.

For sinusoidal wave, form factor

$$K_f = \frac{0.707 I_m}{0.637 I_m} = 1.11$$

It is the ratio of the maximum value to the rms value of an alternating quantity. For a sine wave

$$K_a = \frac{I_m}{I_{rms}} = \frac{I_m}{0.707 I_m} = 1.414$$

Q) The equation of an alternating current is: $i = 62.35 \sin 323t$ A. Determine:

- (i) Maximum value ; (ii) Frequency ;
- (iii) rms value ; (iv) average value ;
- (v) form factor.

Solⁿ: - (i) $I_m = 62.35$ A

(ii) $\omega = 323$

$\Rightarrow 2\pi f = 323$

$\Rightarrow f = \frac{323}{2\pi} = \frac{323}{(2 \times 3.14)} = 51.4$ Hz

(iii) ~~same~~ value RMS value,

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{62.35}{\sqrt{2}} = 44.1$$
 A

(iv) Average value, $I_{av} = \frac{2I_m}{\pi} = \frac{2 \times 62.35}{3.14} = 39.7$


(v) Form factor,

$$K_f = \frac{I_{rms}}{I_{av}} = \frac{41.1}{39.7} = 1.11$$

Phasor or vector Representation of an Alternating Quantity:

The alternating quantities are vectors quantities, i.e., having magnitude as well as direction. However, their instantaneous values are continuously changing. So they are represented by a rotating vector or phasor. A phasor is a vector rotating at a constant angular velocity.

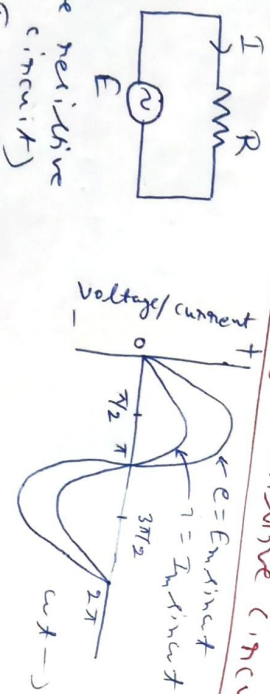The phasor diagram is one in which the same frequency quantities of by phasors with their correct relationship. A phasor diagram represents in one part's clear position of the phasors A.C. through purely resistive circuit:-



(Pure resistive A.C. circuit)
In a circuit containing pure ohmic resistors only, the potential difference across the resistors is

(1) $E = iR$

When $E =$ applied voltage to overcome the ohmic voltage drop only.

$R =$ ohmic resistance

$i =$ instantaneous current

For a.c. circuit,

$E = E_m \sin \omega t$... (2)

From eqns (1) & (2), we get

$iR = E_m \sin \omega t$

$\Rightarrow i = \left(\frac{E_m}{R}\right) \sin \omega t$... (3)

For $\sin \omega t = 1$, the value of current is its max, i.e.,


$I_m = \frac{E_m}{R}$... (4)

From eqns (3) & (4), we get

$i = I_m \sin \omega t$... (5)

From eqns (2) & (5), we see that alternating voltage (E) and alternating current (i) are in phase with each other.

A.C. through purely inductive circuit:-

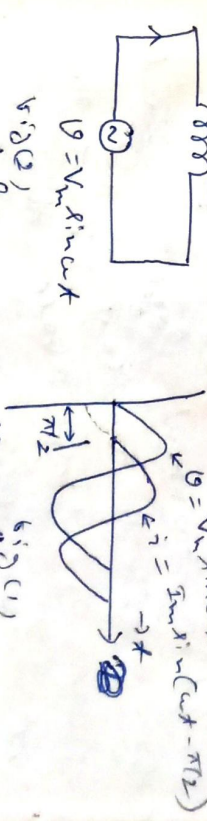

When an alternating voltage is applied to a pure inductive circuit, a back e.m.f. is produced due to the self inductance of the coil. The back e.m.f. at every step opposes the rise on fall of

Current through the coil. Here, the applied voltage lags to overcome the self-induced emf only.

So, at every step,

$$V = L \frac{di}{dt}$$

Now, $V = V_m \sin \omega t$

$$V_m \sin \omega t = L \frac{di}{dt}$$

$$\Rightarrow di = \frac{V_m}{L} \sin \omega t dt$$

Integrating both sides, we get

$$i = \frac{V_m}{L} \int \sin \omega t dt = \frac{V_m}{\omega L} (-\cos \omega t) \text{ (const. = 0)}$$

$$= -\frac{V_m}{\omega L} \cos \omega t \text{ or } i = \frac{V_m}{\omega L} \sin(\omega t - \pi/2)$$

The max value of i when $\sin(\omega t - \pi/2)$ is unity, i.e., $i_m = \frac{V_m}{\omega L}$

Eqn of the current becomes $i = I_m \sin(\omega t - \pi/2)$.

So, the current lags behind the applied voltage by a quarter cycle or the phase difference between the two is $\pi/2$ i.e., voltage leading. In fig (1) & (2) shown in fig (2).

A.C. Through Capacitance Above

If an alternating voltage is applied to the plates of a capacitor, it is charged first in one direction and then in the opposite direction.

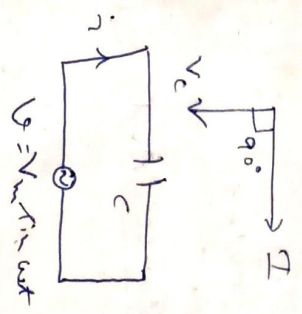


Fig (1)

In the CT diagram given above, let $V = V_m \sin \omega t$ be the voltage across the capacitor. Let $q =$ charge on plates at that instant.

$$Then, q = CV$$

$$= CV_m \sin \omega t$$

The current i is given by the rate of flow of charge.

$$i = \frac{dq}{dt} = \frac{d}{dt} (CV_m \sin \omega t)$$


$$= \omega CV_m \cos \omega t$$

$$\Rightarrow i = \frac{V_m}{\omega C} \cos \omega t = \frac{V_m}{\omega C} \sin(\omega t + \pi/2)$$

$$So, I_m = \frac{V_m}{\omega C} = \omega CV_m \text{ (1)}$$

$$i = I_m \sin(\omega t + \pi/2)$$

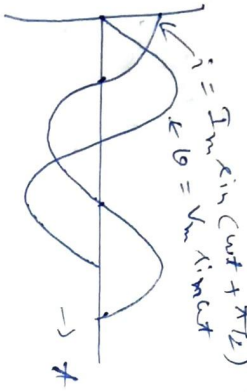Here, $X_C = \frac{1}{\omega C}$ & it is said to be capacitive reactance. The current in a pure capacitor leads the voltage by a quarter cycle.



The vector representation is shown in fig (1) & (2)

A.C. Through Resistance And Inductance In Series


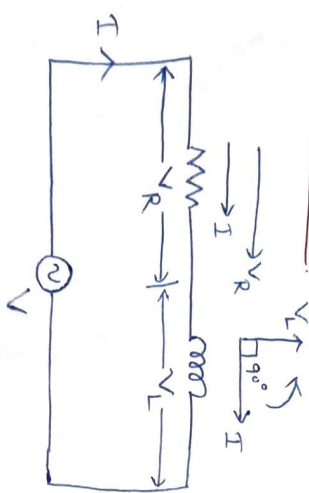


Fig (1) Here, a pure resistance of R ohm and a pure inductive coil of inductance L Henry are connected in series as shown in fig (1). Let $V = V_m \sin \omega t$ value of applied voltage

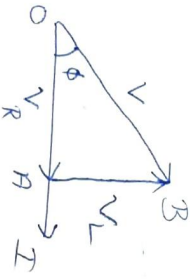

$I = \frac{V_m \sin \omega t}{Z}$ value of resultant current
 $V_R = IR = \text{voltage drop across } R$
 $V_L = IX_L = \text{voltage drop over coil}$
 The voltage drops are shown in the voltage triangle OAB as shown in fig (2)

The vector OA represents ohmic drop V_R . The vector AB represents inductive drop V_L . The applied voltage V is the vector sum of OA and AB. So, the applied voltage is OQ.

$$V = \sqrt{V_R^2 + V_L^2} = \sqrt{(IR)^2 + (IX_L)^2}$$


$$= I \sqrt{R^2 + X_L^2}$$

$$\Rightarrow I = \frac{V}{\sqrt{R^2 + X_L^2}}$$

Here, the quantity $\sqrt{R^2 + X_L^2}$ is said to be the impedance Z of the ckt. The impedance triangle PAM is as shown in fig (3).

Here, $Z^2 = R^2 + X_L^2$
 & $\tan \phi = \frac{X_L}{R}$
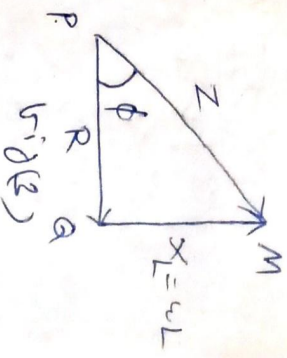
$$\Rightarrow \phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$



The instantaneous values of voltage and current are as shown below in fig (4).

If the applied voltage is $v = V_m \sin \omega t$, then the current eqn is $i = I_m \sin(\omega t - \phi)$ where $I_m = \frac{V_m}{Z}$.



In series:

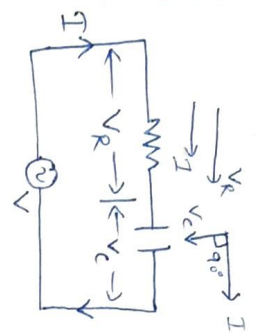


Fig (1)

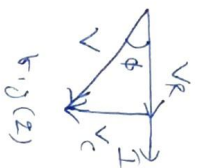


Fig (2)

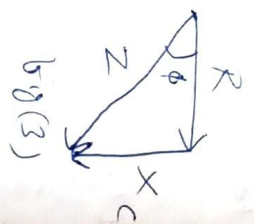


Fig (3)

The ckt diagram is shown in fig(1).
Here, $V_R = IR = \text{drop across } R$

$V_C = IX_C = \text{drop across Capacitor}$
Since Capacitive reactance X_C is taken negative, V_C is along negative direction of Y-axis. IX_C is shown in fig (2).
Now, $V = \sqrt{V_R^2 + V_C^2}$

$$\Rightarrow I = \frac{V}{\sqrt{R^2 + X_C^2}} = \frac{V}{\sqrt{(IR)^2 + (-IX_C)^2}}$$


The impedance triangle is shown in fig (3).

tan $\phi = \frac{X_C}{R}$

It is the eqn of the alternating voltage is the applied voltage in the circuit in the current in the circuit.

$i = I_m \sin(\omega t + \phi)$

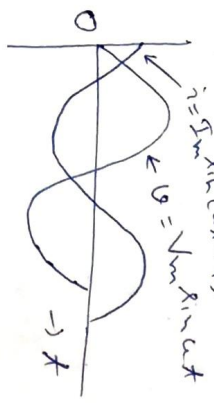Here, the current leads the applied voltage by an angle ϕ . The instantaneous values of voltage and current are shown below in fig (4).



Resistance, Inductance and Capacitance in series:

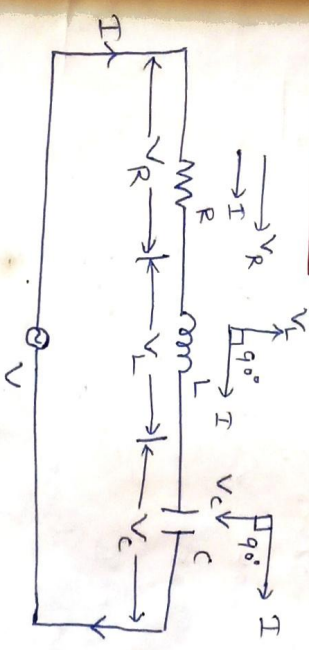


Fig (1)

In the above ckt diagram, a.c. supply of rms. Voltage V is applied across resistor, inductor & capacitor connected in series.

Let $V_R = IR = \text{voltage drop across } R$.

$V_L = IX_L = \text{voltage drop across } L$.

$V_C = IX_C = \text{voltage drop across } C$.

The voltage triangle is shown in fig. (2) & the impedance triangle is shown in fig (3) below.

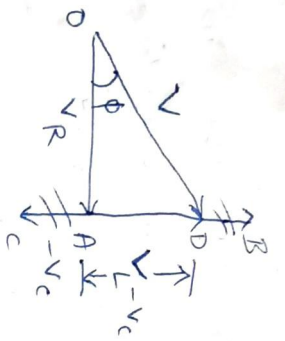


Fig (2)

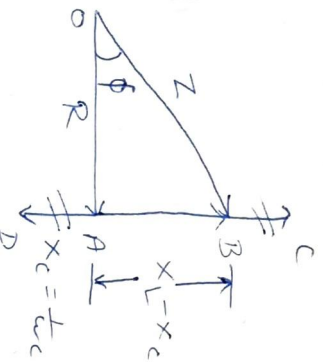


Fig (3)

In voltage triangle, OD represents V_R , AB is inductive drop and AC is capacitive drop. Here, V_L & V_C are 180° out of phase with each other. V_L is taken greater than V_C in magnitude in this case. By subtracting BD from AB, we get the net reactive drop $AD = V_L - V_C = I(X_L - X_C)$ The applied voltage V is OD and in the vector sum of OD and AD.

$$OD = \sqrt{OR^2 + AD^2}$$

$$\Rightarrow V = \sqrt{(IR)^2 + (IX_L - IX_C)^2}$$

$$= I \sqrt{R^2 + (X_L - X_C)^2}$$

$$\Rightarrow I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{V}{Z}$$

In the impedance triangle

$$Z^2 = R^2 + (X_L - X_C)^2 = R^2 + X^2$$

where, $X =$ net reactance the phase angle ϕ is

$$\tan \phi = \frac{X_L - X_C}{R} = \frac{X}{R}$$

In the eqn of the applied voltage is $V = V_m \sin \omega t$, the eqn of the resulting current is $i = I_m \sin(\omega t \pm \phi)$

The 'true' sign is taken when current leads, i.e., when $X_C > X_L$. The '-ve' sign is taken when current lags, i.e., when $X_L > X_C$.

Power Factor: - It is defined as


cosine of the angle of lead or lag betⁿ the rms. value of supply voltage and the rms. value of resultant current. It is also defined as the ratio

$$\frac{R}{Z} = \frac{\text{Resistance}}{\text{Impedance}} \text{ on the ratio } \frac{W}{VA} = \frac{\text{watts}}{\text{volt. ampere}} = \frac{\text{true power}}{\text{apparent power}}$$

Power Triangle: -

Suppose a series R-L ckt draw a current of I

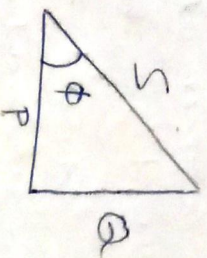when an alternating voltage of rms. value V is applied to it. So, current lags behind the applied voltage



lags behind the applied voltage

Then, the three powers drawn by the CKT is as follows.

① Apparent Power (S): $-I + j$, is the product of r.m.s. value of applied voltage and CKT current.

$S = VI = (IZ)I = I^2Z$ Volt-ampere

② Active Power (P or W): $-IT$, is the power which is actually dissipated in the CKT resistance.

$P = I^2R = VI \cos \phi$ Watts.

③ Reactive Power (Q): $-IT$ is the power developed in the inductive reactance of the CKT.

$Q = I^2X_L = VI \sin \phi$ Volt-ampere reactive


The three powers are shown in the power triangle in the diagram.

In the power triangle, $S^2 = P^2 + Q^2$

$\Rightarrow S = \sqrt{P^2 + Q^2}$

Complex Notation Applied To A.C. Circuits -

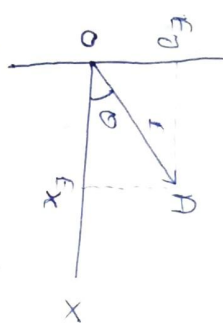In complex algebra method, a phasor is resolved into two components (complex notation) at right angle to each other.



Let's consider the phasor E, represented in magnitude, and direction by OA.

Then, $E^2 = E_x^2 + E_y^2$

The phasor E can be represented in Cartesian form as $E = E_x + jE_y = E(\cos \theta + j \sin \theta)$

The symbol $j (= \sqrt{-1})$ represents an operator indicating the anticlockwise rotation of phasor through 90° . In polar method of representation, the phasor E can be written symbolically as $\vec{E} = |\vec{E}| \angle \theta$.

where $\theta = \tan^{-1} \left(\frac{E_y}{E_x} \right)$

$|\vec{E}| = \sqrt{E_x^2 + E_y^2}$

Generation of Electrical Power

Hydro electric power stations -

In the hydroelectric power station, the potential energy of water head is used to generate electrical energy. The water head is created by constructing a dam across a river. The water from the dam is taken to the water turbine through valve house with the help of steel pipe known as penstock. The large tank protects

in case of turbine gates suddenly get closed. The turbine converts hydraulic energy into mechanical energy. The alternator connected to the turbine converts the mechanical energy into electrical energy.



Dam - A dam is a barrier which stores water and creates which head. Dams are built of concrete or stone on rock hill.

Surge tank - When the closed conduits are used, then there is always provided a surge tank. A surge tank

a small reservoir on tank in which water level rises or falls to reduce the pressure swings in the conduit.

Valve house - The valve house contains main sluice valves and automatic isolating valves. The governor controls the water flow to the power house and the auto isolating valves cut off the supply of water when the penstock bursts.

Advantages - 1) It requires no fuel as water is used for the generation of electrical energy.

2) It is quite neat and clean as no smoke or ash is produced.

3) It requires less maintenance.

4) It is robust and longer life.

5) In addition to the generation of electric energy, they also help in irrigation and controlling floods.

Disadvantages - 1) It involves high capital cost due to the construction of dam.

2) There is uncertainty about the availability of large amount of water.

Nuclear Power Station

A generating station in which nuclear energy is converted into electrical energy is known as a nuclear power station.



In nuclear power station, heavy elements such as Uranium, heavy

Or Thorium (Th_{232}) or Plutonium (Pu_{239}) are subjected

to nuclear fission in a special apparatus known as a reactor. Nuclear fission —

The splitting of heavy nucleus into two or more smaller nuclei, with release of large amount of energy is known as nuclear fission.

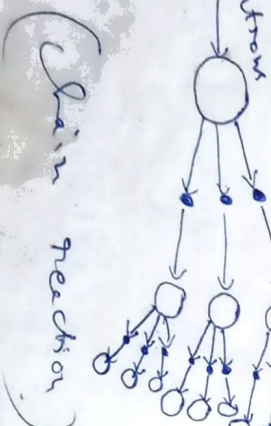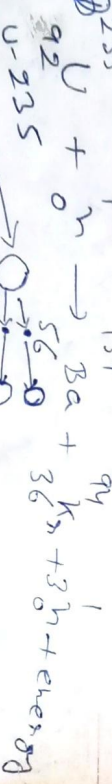
In the nuclear fission process, the heavy nucleus is bombarded by the slow neutrons.




(Chain reaction)

The heat energy thus released is utilized in raising steam at high temp. & pressure. The steam runs the steam turbine which converts steam energy into mechanical energy. The turbine drives the alternator which converts mechanical energy into electrical energy. The most important feature of a nuclear power station is that large amount of electrical energy can be produced from a small amount of nuclear fuel.

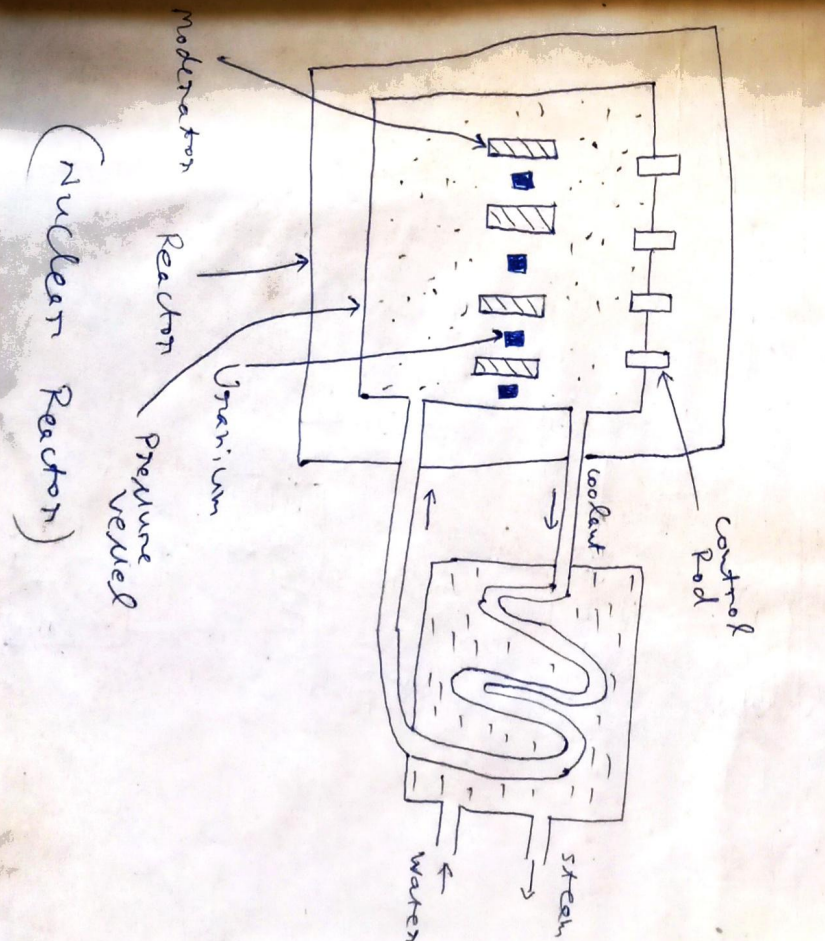Schematic Arrangement of Nuclear Power Station



(Nuclear Reactor)

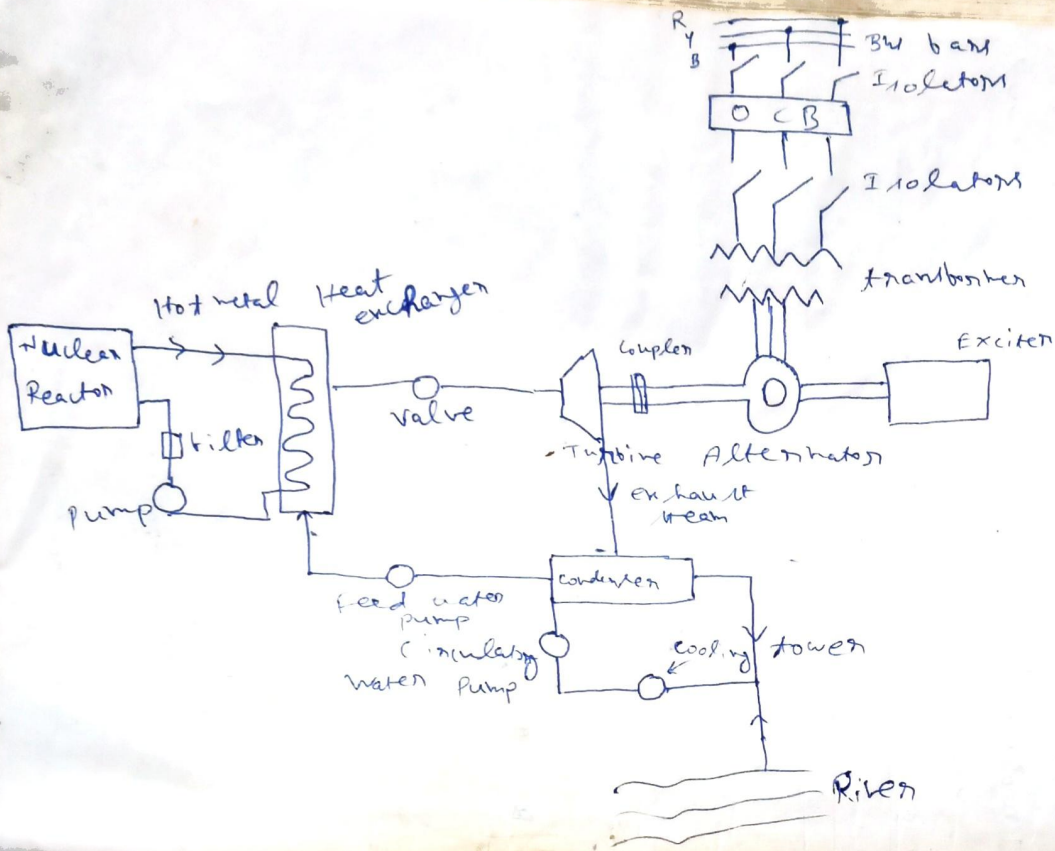

A nuclear power plant consists of a nuclear reactor (for heat generation), heat exchanger (for converting water into steam by using the heat generated in nuclear reactor), steam turbine, alternator, condenser, etc.

The huge amount of heat energy produced in breaking of atoms of uranium or other similar metals of large atomic weight into lower atomic weight by fission process. The heated metal or gas is then allowed to exchange its heat to the heat exchanger by circulation. In the heat exchanger the water is heated and steam is generated which is utilized to drive the turbine coupled to an alternator thereby generating electrical energy.

Main parts of Nuclear Power plant:
Nuclear Reactor: -

It is an apparatus in which the nuclear fuel (^{235}U) is subjected to nuclear fission. It controls the chain reaction. If the chain reaction is not controlled the result will be an explosion.

due to the built increase in the energy released.

A nuclear reactor is a cylindrical pressure vessel and houses of fuel rods of uranium, moderator and control rods.

→ The fuel rods capture the fission material and release huge amount of energy when bombarded with slow moving neutrons.

→ The moderator slows down the neutrons before they bombard the fuel rods. For moderator, Carbon, Heavy water, ordinary water is used.

→ Control rods are meant for controlling the rate of fission of U^{235} . There are made of Boron-10, Cadmium or

Plutonium and are inserted into the reactor. It is used to absorb the neutrons & regulate the supply of neutrons to fission.

→ The heat produced in the reactor is removed

by the coolant, generally a sodium metal (metal), Air, Hydrogen, CO_2 (gas), Light and heavy water (liquid). The coolant carries the heat to the heat exchanger.

(i) Heat Exchanger: - The coolant gives up heat to the heat exchanger which is utilized for producing the steam.

(ii) Steam turbine: - The steam produced in the heat exchanger is passed through the steam turbine. After doing the useful work in the turbine, the steam is exhausted to condenser. The condenser condenses the steam which is fed to the heat exchanger.

(iii) Alternator: - The steam turbine drives the alternator which converts the mechanical energy into electrical energy. The output from the alternator is delivered to the bus-bars through the transformers.

Advantages: - ① The amount of fuel required is less.

② Less space is required.

③ Very economical for producing bulk electrical power.

④ It has low running charges.

Disadvantages: - ① The fuel used is expensive.

② The capital cost is high.

③ The by-products are generally radioactive and may cause the radioactive pollution.

④ Maintenance charges are high.


Thermal Power Station

A generating station which converts heat energy of coal combustion into electrical energy is known as a steam power station.

Steam is produced in the boiler by utilizing the heat of coal combustion. The steam is then expanded in the prime mover and condensed in the condenser to be fed into the boiler again. The steam turbine drives the alternator which converts the mechanical energy of turbine into electrical energy. This is type of energy.

Power station is suitable where coal & water are available plentifully and a large amount of electrical power is to be generated.

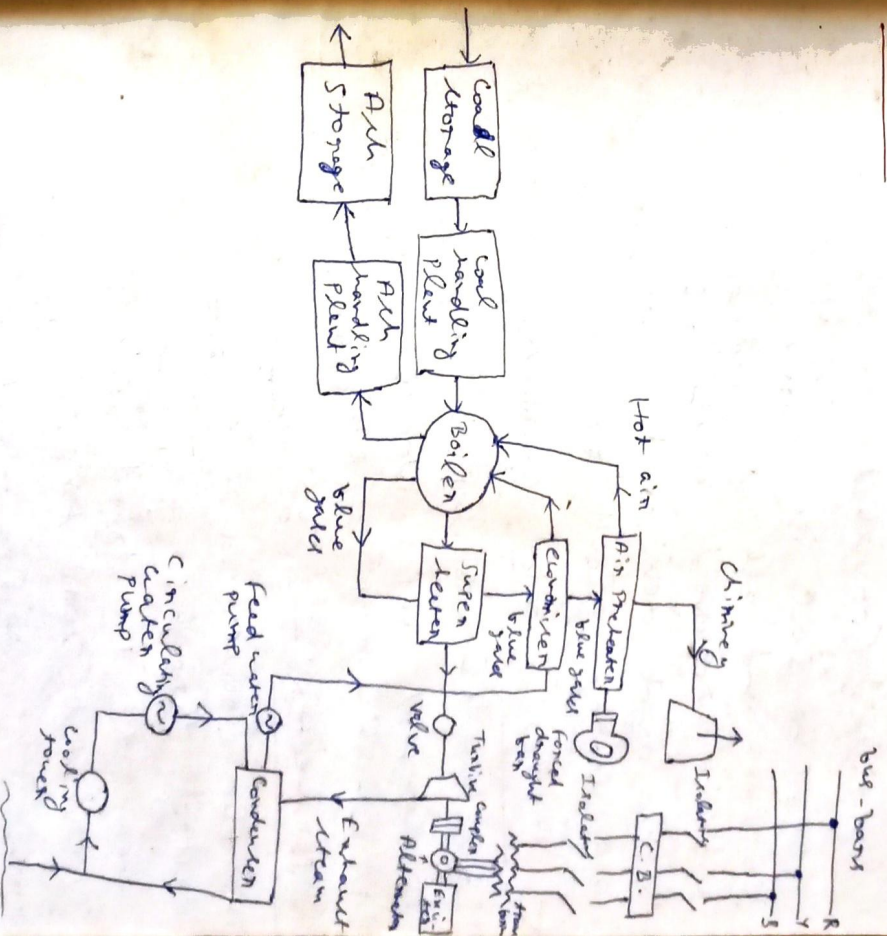Schematic Arrangement of steam power station



The whole arrangement can be divided into the following stages.

- ① Coal and ash handling arrangement.
- ② Steam generating plant.
- ③ Steam turbine.
- ④ Feed water cooling arrangement.

- ① The coal is transported to the power station by rail or road
- (and is stored in the coal storage plant. From the coal storage plant, coal is delivered to the coal handling plant when it is pulverised (crushed into small pieces).

The coal is burnt in the boiler and air is produced. The air is removed to the air handling plant and delivered to the air storage plant for disposal.

② Boiler: - The combustion of coal in the boiler is utilized to convert water into the steam at high temp. & pressure.

Superheater: - The steam produced in the boiler is set and is passed through a superheater where it is dried and is superheated (steam temp. increased above the boiling point of water) by the blue gases or the way to chimney.

Economiser: - It is a bed of water heaters and economiser heat from the blue gases.

to the economiser before supplying to the boiler. The economiser extracts a part of heat of blue gases to increase the feed water temp.

Air Preheater: - It increases the temp. of the air supplied for coal burning by deriving heat from blue gases.

③ The dry and superheated steam from the superheater is led to the steam turbine through main valve. When steam is passing over the blades of turbine the heat energy of steam is converted into mechanical energy. After giving heat energy to the turbine, the steam is exhausted to the condenser that condenses the exhausted steam by means of cold water circulation.

④ Feed water: - The condensate from the condenser is used as feed water to the boiler. The feed water on its way to the boiler is heated by water heaters and economiser.

⑤ Cooling arrangement: - The water is drawn from a river & is circulated through the condenser.

The circulating water rises up the heat or the exhausted steam and becomes hot. Then the hot water going out from the condenser is discharged at a suitable location down the river. If water is not available in the river, then cooling towers are used. The hot water from the condenser is pumped on to the cooling towers where it is cooled. Then the cold water from the cooling towers is reused in the condenser.

Advantages: -

- ① The fuel used is cheap.
- ② The initial cost is less as compared to other generating stations.
- ③ It can be installed at any place irrespective of the existence of coal.
- ④ As compared to the hydroelectric power station, less space is required.

Disadvantages: -

① It pollutes the atmosphere because of the production of large amount of smoke & large amount of CO_2 compared to hydroelectric plant.

Measuring Instruments

Introduction: - The various electrical instruments are divided into two types. ① Absolute instruments & ② Secondary instruments.

Absolute instruments: - The instruments that give the value of the quantity to be measured in terms of the constant of the instrument and their deflection only.

Secondary instruments: - The instruments in which the value of electrical quantity to be measured can be determined from the deflection of the instruments only when they have been pre-calibrated by comparison with an absolute instrument. Another way of classifying secondary instruments are (a) indicating instruments, (b) recording instruments, (c) integrating instruments.

Indicating instruments: - The instruments that indicate the instantaneous value of the electrical quantity being measured at the time at which it is being measured.

Their indications are given by pointers moving over calibrated dials.

Recording instruments: - The

1. Instruments that give a continuous record of the variations of such a quantity over a selected period of time.
2. Integrating instruments: - the instruments that measure and register by a set of dials and pointers either the total quantity of electricity or the total amount of electrical energy supplied to a circuit in a given time.

Torques in instruments

Deflecting Torque: - The deflecting torque causes the moving system to move from its zero position. Controlling Torque: - It serves to control the moving torque, the deflection of the moving system would be indeterminate. The torque opposes the deflecting torque and increases with the deflection of the moving system. The pointer is brought to rest when

the two opposing torques are equal.

Damping Torque: - The damping torque acts on the moving system of the instrument only when it is moving and always opposes its motion.


Different use of PMMC type of instruments:

1. It has low power consumption.
2. It is modified with the help of shunts and resistances to cover a wide range of currents and voltages.
3. As the operating fields of such instruments are very strong, they are not much affected by stray magnetic fields.
4. It is widely used for d.c. work.
5. It can be used as ammeters with the help of a low resistance shunt.
6. It can be used as voltmeters with the help of a high series resistance.



Different use of MT type of instruments:

1. It can be used both on a.c. & d.c. circuits.

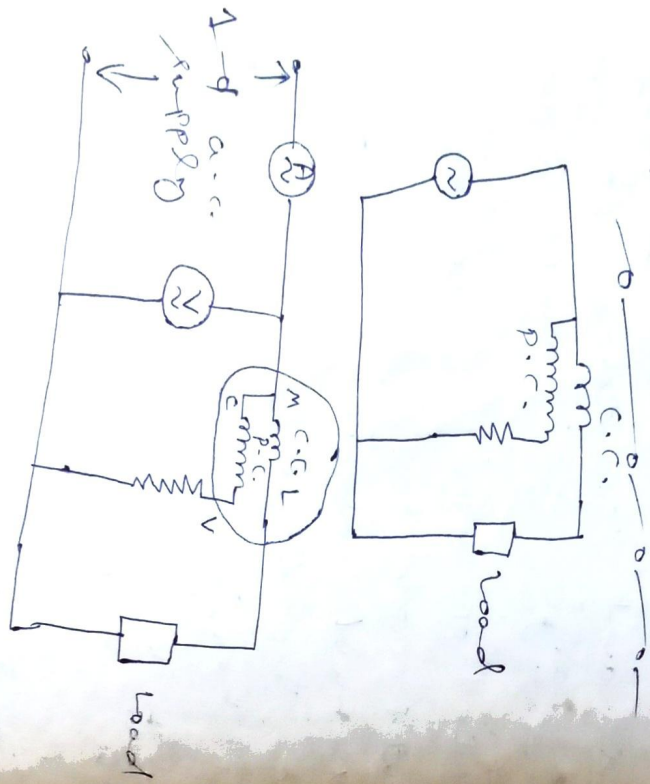- 2) The range of the moving-instrument as ammeter can be extended by using a suitable shunt across its terminals.
- 3) The range of the instrument can be extended by using a high non-inductive series resistance connected in series with it.



In this system of internal wiring, cables are supported and gripped by porcelain cleat 1cm above the wall or ceiling. The porcelain cleats are made in two halves. The main part is base that is grooved to accommodate the cable and the cap is put over it. The lower cleat and upper cover often playing cables both them are then screwed on wooden plugs (goggles). The goggles previously fixed into wall or ceiling at regular interval should be 30cm to 60cm apart.

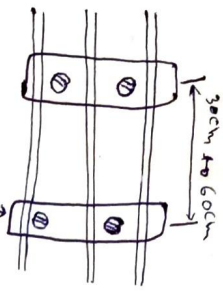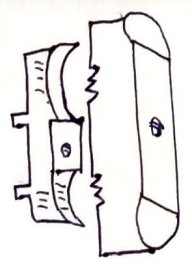

Advantages: -

- 1) Its installation and dismantling is easy and quick.
- 2) The inspection work is easy as the cables are cut in right.
- 3) The installation is very cheap and the material often dismantlement is recoverable for re-use.
- 4) An unskilled electrician can do the job.